

LECTURE I

Introduction to Electrical Engineering and Embedded Systems

SECTION I

What is an Embedded System?

Embedded Systems

- An **embedded system** is a combination of hardware and software designed for a specific purpose
 - Ex) alarm clock, camera, or MP3 player



- Contrasts from a **general-purpose system**, like a smartphone or laptop
 - These devices can act as an alarm, camera, and a media player *combined*
 - They typically have much more functionality than an embedded system

What are some more **examples** of embedded systems?



Embedded Systems

- Large-scale mechanical and electrical systems often consist of **multiple, smaller embedded systems**
 - Each embedded system has a function that supports the larger system
 - Ex) **Airplanes** - in-flight entertainment system, temperature control, speed control, flight management, flight data recorder



Embedded Systems

- In **Lecture IV**, we discuss the architecture of embedded systems in the context of Arduino
- For now, we will focus on the physics and circuits principles that embedded systems rely on...




SECTION II

The Science of Electric Circuits

Energy


- **Energy** is the ability to do work
 - In physics class, you learned about potential and kinetic energy
 - **Potential energy** represents the energy stored in an object that has the *potential* to become another form of energy (usually kinetic)
 - **Kinetic energy** is the energy associated with an object's motion
 - Mechanical motion
 - Radiation/light emission
 - Electron flow
 - **Work** is the *change* in kinetic energy in a system; work creates motion

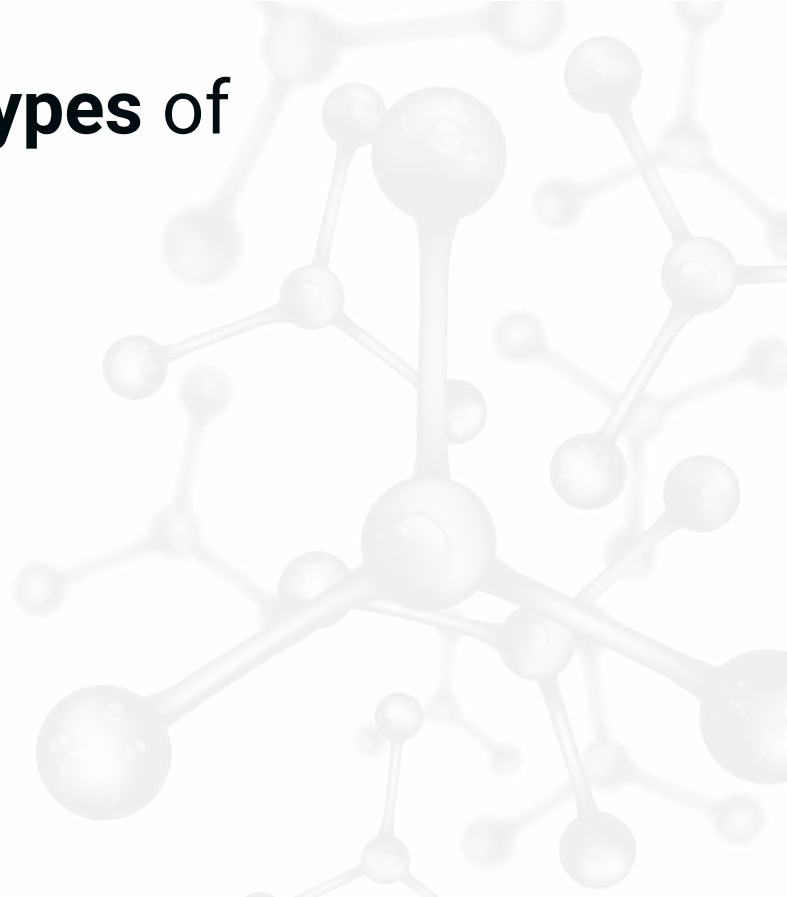What are some of the **different types** of potential/kinetic energy?



Entropy

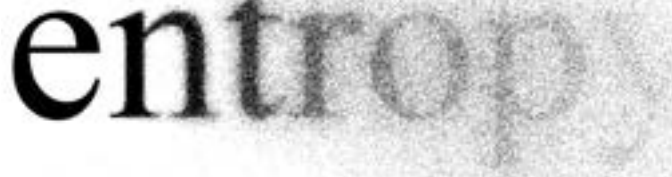
- **Nature favors systems with higher entropy**, which increases stability
- In stable systems, **energy is more *randomly* distributed**
 - The **potential energy** of bodies in the system **is reduced and disbursed** as other forms of energy (like thermal energy)



entropy

Electricity

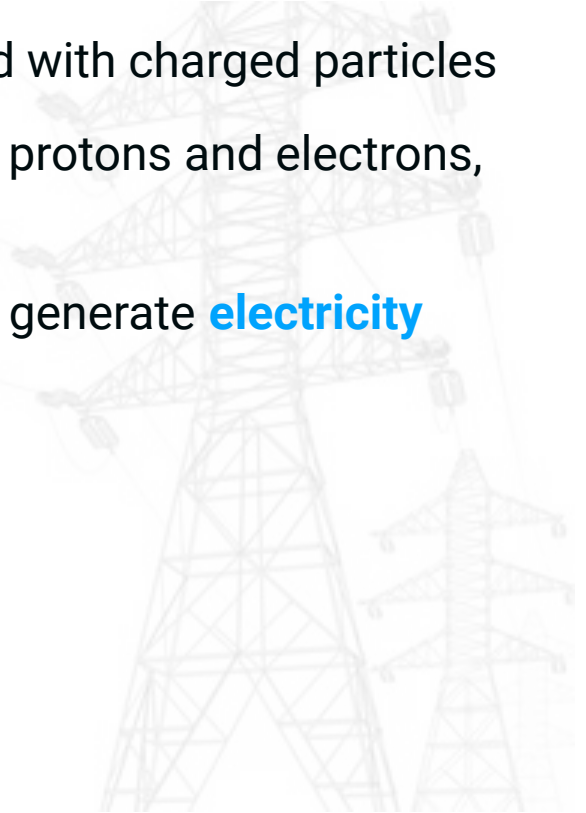
- We focus on **electrical energy** - the energy associated with charged particles
 - Charged particles include (but are not limited to) protons and electrons, but we are concerned only with **electrons**
 - Still electrons are boring, but electrons in motion generate **electricity**



Current

- **Current** is the flow of charged particles, usually electrons
 - Current has a magnitude **Amperes (A)** and direction
 - **Conventional current** flows in the direction *opposite* to the electron flow

**Conventional
Current**

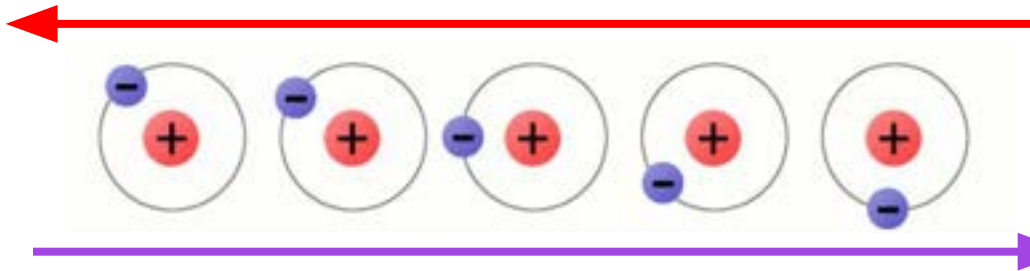

Electron Flow

- But what generates current?

ELECTRIC POTENTIAL

- **Electric potential** is the amount of work needed to move a charged particle between two points
 - Measured in **Volts, V**
- Charged particles move from points of higher electric potential to points of lower electric potential (remember entropy?)
 - ... this means that electron flow - **current** - is **generated when there is a difference in electric potential** between two points

Voltage

- **Voltage** is the **electric potential difference**
 - Current can flow where **voltage** exists
 - Measured in **Volts, V**
- **Batteries** are a voltage source
 - Current will flow from the **positive (+)** terminal to the **negative (-)** terminal when connected
 - The **positive (+)** terminal has a *higher* potential than the **negative (-)**



Voltage

- **Measuring voltage requires a reference point** ← called “Ground”/”GND”
because it is the difference in volts between two points
- Using the **negative (-)** terminal of the battery as a reference point...
 - The **positive (+)** terminal has a **voltage** of **+9V**
 - The **negative (-)** terminal has a **voltage** of **+0V**
 - **Why zero?** There is no potential difference at the same location as the reference point





Conductors

- Current cannot flow without a path for the electrons to move
- A **conductor** is a material in which electrons can move freely
 - If a **voltage** exists across a conductor, current will flow
- Common conductors include:
 - **Copper**
 - Gold
 - Silver
 - Aluminum



Resistors

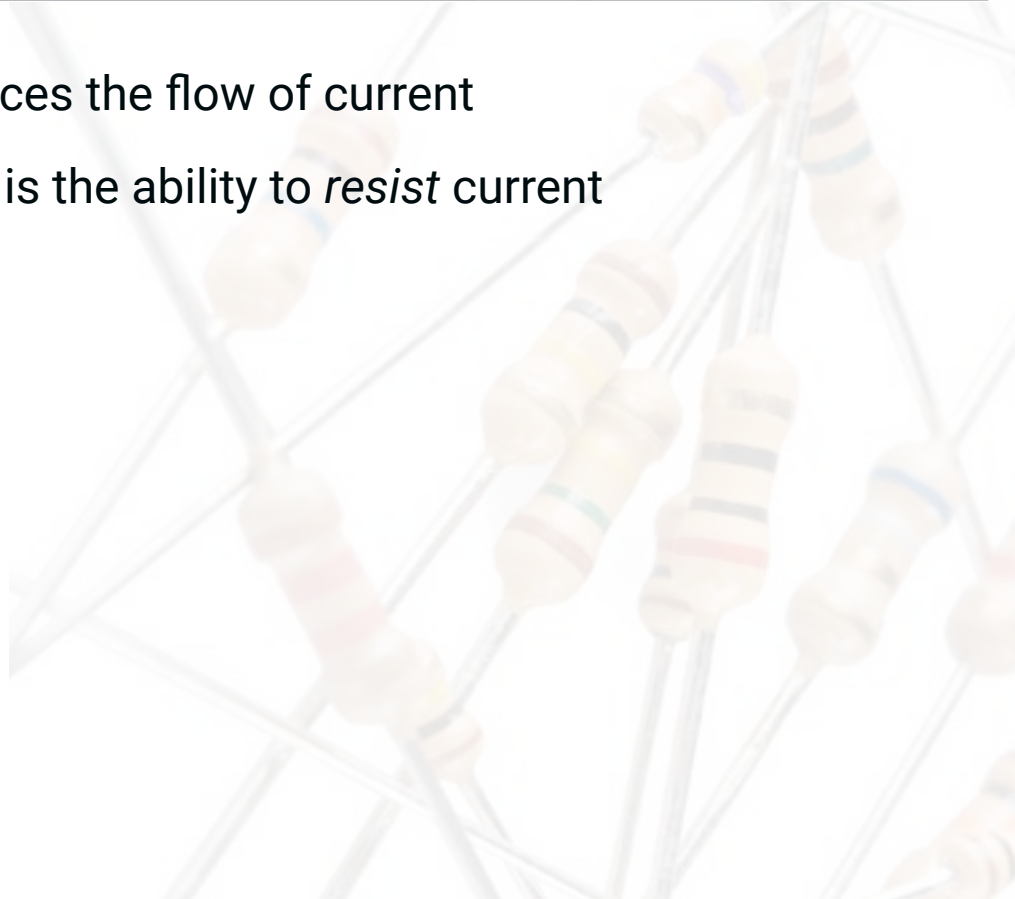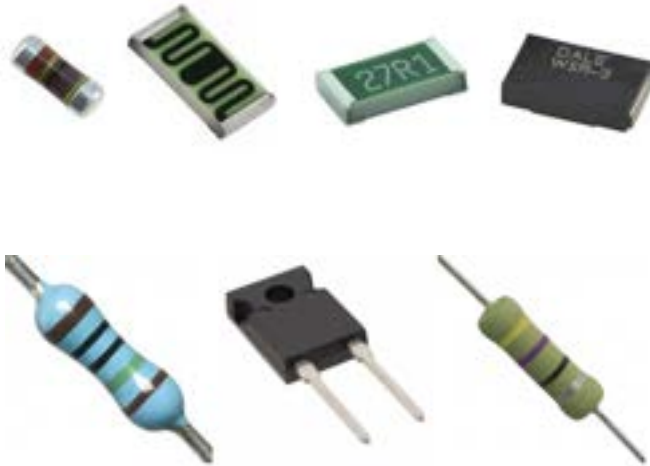- A **resistor** is a component that reduces the flow of current
- **Resistance**, measured in **ohms (Ω)**, is the ability to *resist* current



Circuits


- A **circuit** is a **closed loop** path where electrons can flow
- An **open circuit** contains a **discontinuity** that disrupts the current flow
 - Ex) An open switch on a circuit prevents current from flowing
- A **closed circuit** has a **fully continuous** path for current to flow through



Ohm's Law

$$V = IR$$

- Relates the **voltage (V)**, **current (I)**, and **resistance (R)** in a circuit
- Suppose we hold the voltage at a constant value:
 - As the resistance increases, current decreases
 - In the opposite case, as resistance decreases, current increases

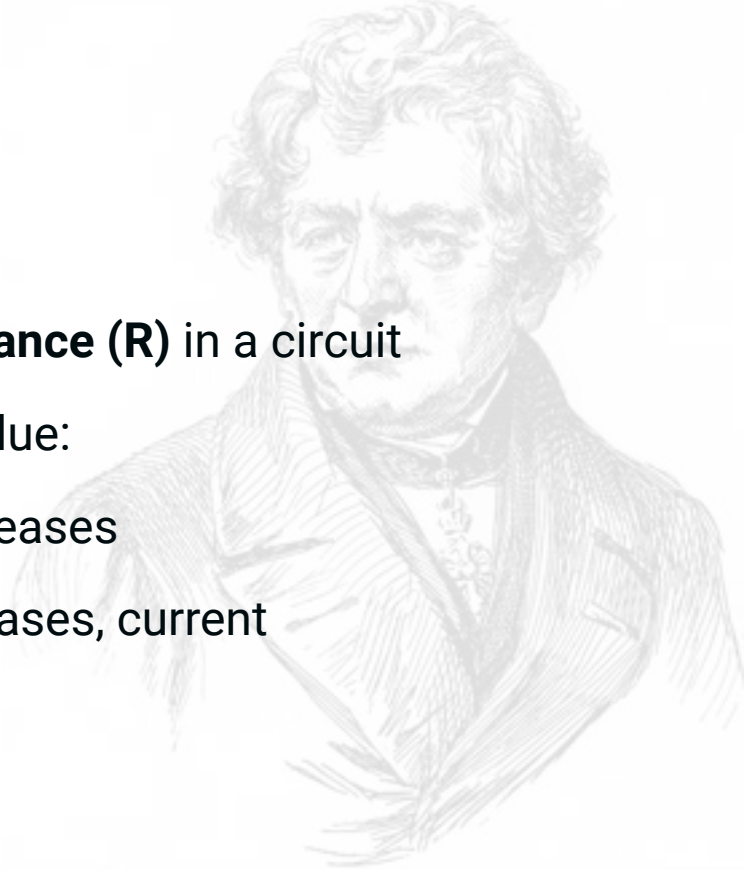

SECTION III

Building DC Circuits


AC/DC Circuits

- This course's projects focus on **direct current (DC)** circuits where the **voltage and direction of current is constant**
- Other circuits rely on **alternating current (AC)** where the **current's direction oscillates** back and forth

Direct Current



Alternating Current

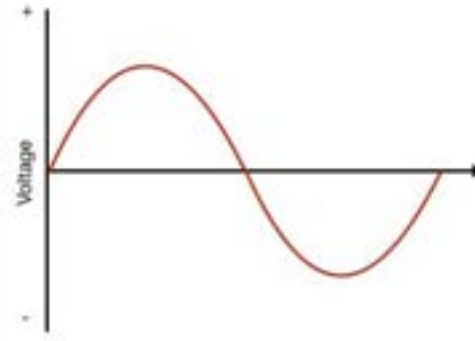

Circuit Components


- All circuits require the following three components:
 - A **voltage source** to provide electrical energy and generate current
 - Ex) DC generators, batteries, solar cells
 - A **conductive path** for current to flow
 - Ex) wire, circuit board traces, occasionally air (lightning)
 - A **load** to expend the electrical energy
 - Ex) light bulbs, sound speakers, motors, occasionally you

Polarized Components


- A **polarized component** is one which can only be **connected** to the circuit **in one direction**
 - Ex) Batteries, LEDs, Electrolytic Capacitors
 - These components have a **positive (anode)** and **negative (cathode)** terminal
 - Remember that current flows from **positive** to **negative**
 - Terminals may be **distinguished by lead length, labels, or notches** on the component
 - Sketches of circuits will also indicate the components' polarities

LEDs

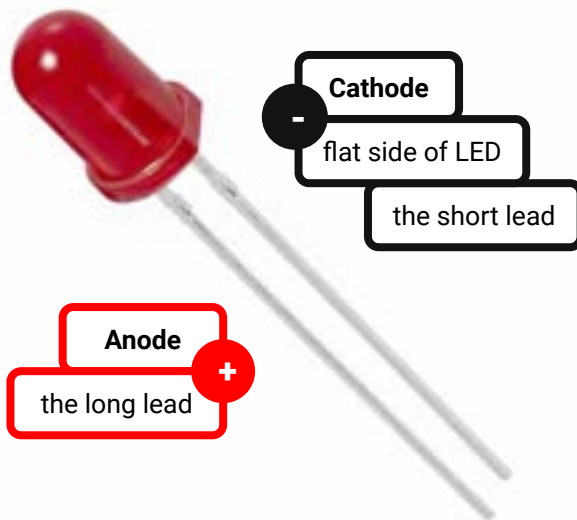
- The **Light Emitting Diode (LED)** is a component that emits light (big surprise)
 - As a **diode**, the LED is **polarized** and has a constant **forward voltage** between its anode and cathode terminals (in normal operating conditions)
 - Refer to the LED's **datasheet** to find its **operating conditions**
 - Recommended operating current
 - Forward Voltage



Datasheets

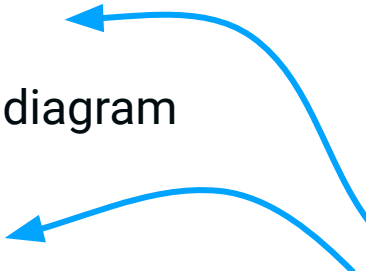- The manufacturer of a component or device creates a **datasheet** to document its **characteristics** and **operating conditions**
 - Common features of a datasheet:
 - **Summary**
 - Functional block diagram or schematic diagram
 - Pinout
 - **Recommended operating conditions**
 - Graphs
 - Truth Tables
 - Timing Diagrams
- 
- We will only focus on these two features today

Datasheets

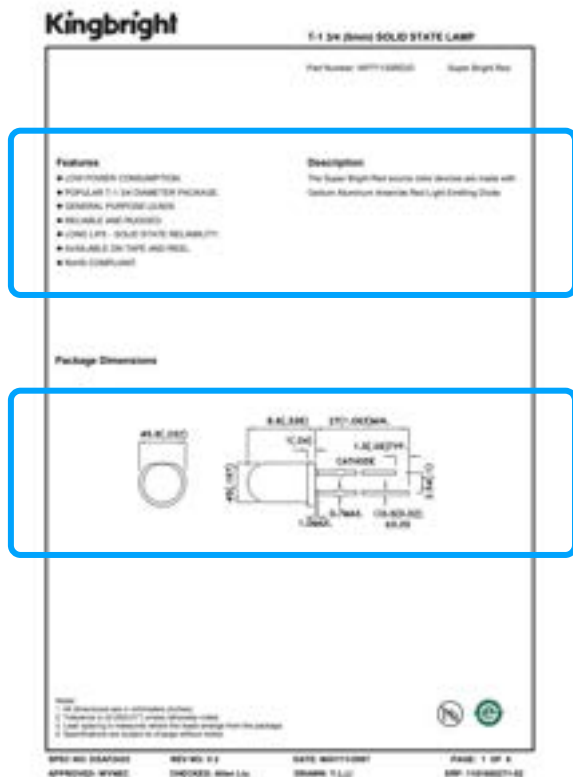

Summary

- The first page of a datasheet is often a **summary** of the device
- It contains a **description** of the device and its **features**
- It may also include a **high level schematic** of the device and its **dimensions**

Datasheets

Kingbright

Selection Guide				
Part No.	Desc.	Case Type	In Stock (2)	
			Min.	Typ.
SRHT-100000	Super Bright Red (2pin)	SRHT-100000	100	200

Note:

1. LED is the suggested optical wavelength when the ambient intensity is 10 lux or higher.

2. Led-on-time: 100ms, duty: 10%.

Electrical / Optical Characteristics at Ta=25°C

Symbol	Parameter	Device	Typ.	Min.	Max.	Test Conditions
I_f	Forward Current	Super Bright Red	400	100	1000	$V_f=2.0V$
I_{RM} (1)	Reverse Maximum	Super Bright Red	100	100	1000	$V_R=5V$
I_{AV} (2)	Average Current	Super Bright Red	10	10	100	$V_f=2.0V$
I_{P}	Pulse Current	Super Bright Red	40	10	1000	$V_f=2.0V$
V_f (3)	Forward Voltage	Super Bright Red	1.80	1.5	2.2	$I_f=10mA$
R_f	Resistance (typical)	Super Bright Red	10	10	10	$V_f=2.0V$

Note:

1. Reverse current: 100mA.

2. Forward voltage: 1.8V.

Absolute Maximum Ratings at Ta=25°C

Parameter	Super Bright Red	Unit
Power dissipation	10	mW
LED Forward Current	100	mA
Peak Forward Current (1)	100	mA
Reverse Voltage	5	V
Operating Temperature	-40°C to +85°C	
Lead Solder Temperature (2)	260°C for 10 seconds	
Lead Solder Temperature (3)	260°C for 10 seconds	

Note:

1. 100% duty cycle, 100% power.

2. 100% duty cycle, 100% power.

3. 100% duty cycle, 100% power.

SRHT-100000

REV 001 V1.0

DATE: 2017/10/27

PAGE: 1 OF 1

APPROVED: 01/01/2017

CHECKED: 01/01/2017

DESIGN: 01/01/2017


SRHT-100000-01

Recommended Operating Conditions

- This section of the datasheet usually contains a **suggested current and/or voltage** as input to the device
- **Absolute maximum ratings** are the limit for operating the device safely
 - Use reasonably lower values than ones listed as the maximums

Resistor Bands

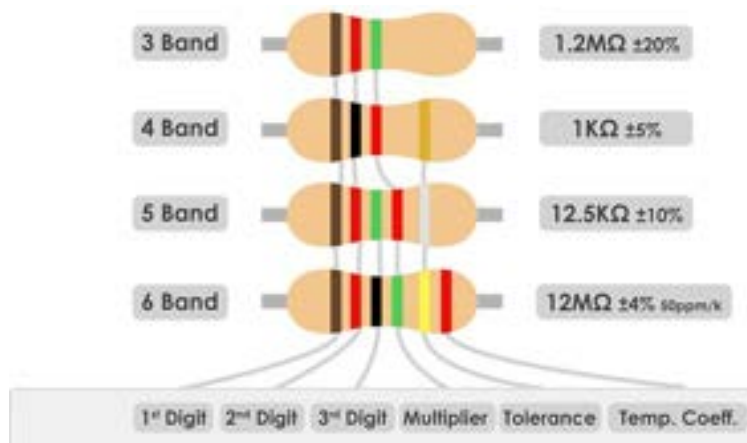
- The **resistance** of many **axial resistors** (which have a lead at either end of the resistor) can be determined using their **colored bands**



	1 st Digit	2 nd Digit	3 rd Digit	Multiplier	Tolerance	Temp. Coeff.
Black	0	0	0	$\times 10^0$		250 (U)
Brown	1	1	1	$\times 10^1$	$\pm 1\%$	100 (S)
Red	2	2	2	$\times 10^2$	$\pm 2\%$	50 (R)
Orange	3	3	3	$\times 10^3$	$\pm 3\%$	15 (P)
Yellow	4	4	4	$\times 10^4$	$\pm 4\%$	25 (Q)
Green	5	5	5	$\times 10^5$	$\pm 0.5\%$	20 (Z)
Blue	6	6	6	$\times 10^6$	$\pm 0.25\%$	10 (Z)
Violet	7	7	7	$\times 10^7$	$\pm 0.1\%$	5 (M)
Grey	8	8	8	$\times 10^8$	$\pm 0.05\%$	1 (K)
White	9	9	9	$\times 10^9$		
Gold	-	-	-	$\times 10^{-1}$	$\pm 5\%$	
Silver	-	-	-	$\times 10^{-2}$	$\pm 10\%$	

Schematics

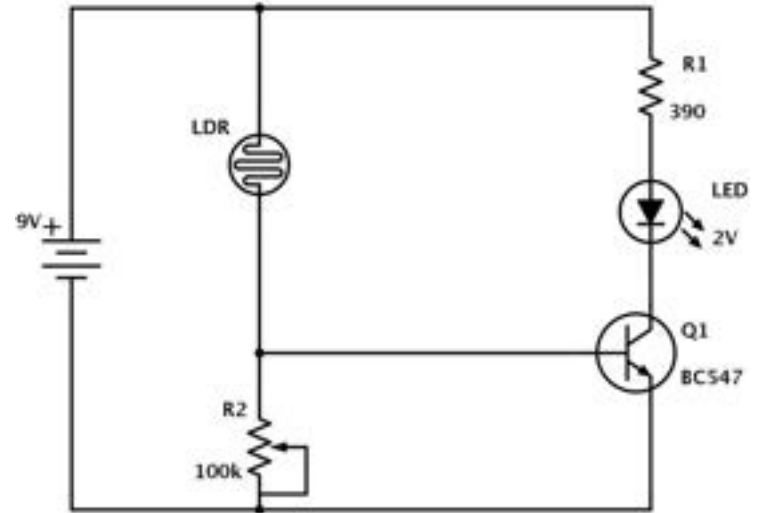- A **schematic** diagram defines the **connections between components** in a circuit
- Schematics also **summarize the components' values**
- Each component has a **unique symbol** associated with it



Schematic Symbols

Battery



Voltage Source



Ground



Resistor



Potentiometer



Switches




Pushbutton



Speaker



DC Motor

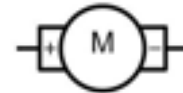


LED




Schematic Connections

Connected Wires

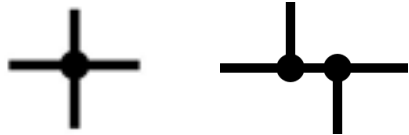



Unconnected Wires

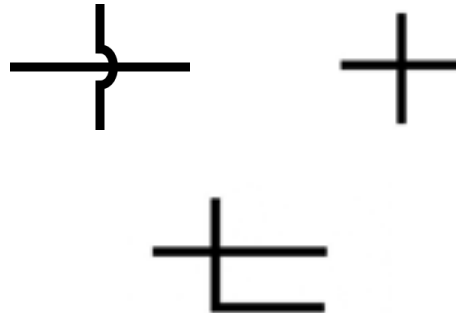

Applying Ohm's Law


I/A

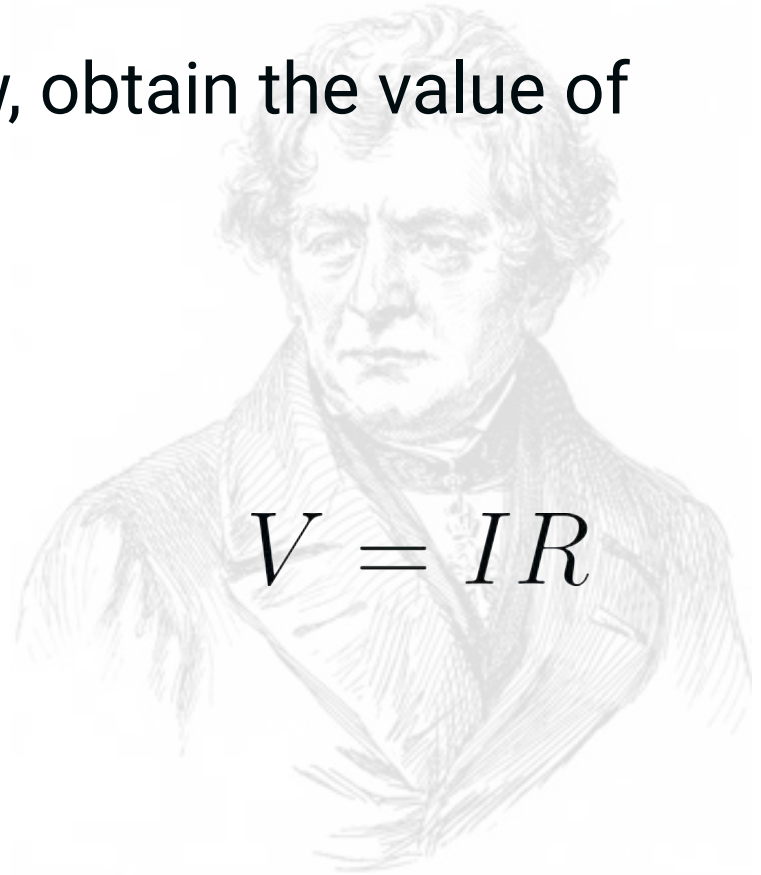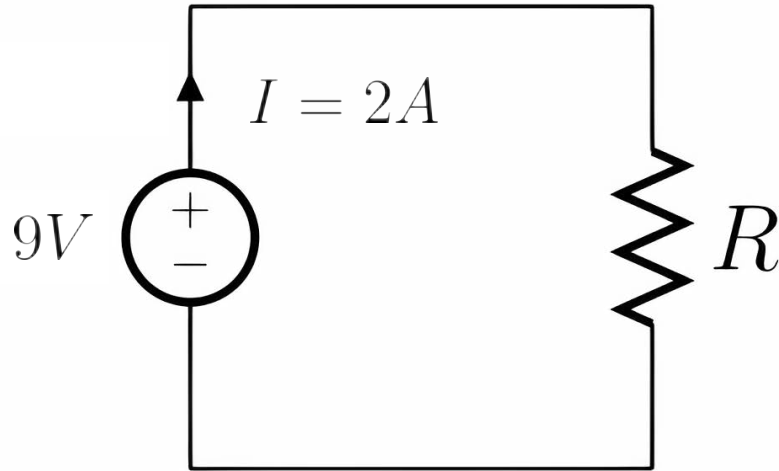Given the circuit schematic below, obtain the value of resistor (**R**).




Breadboards

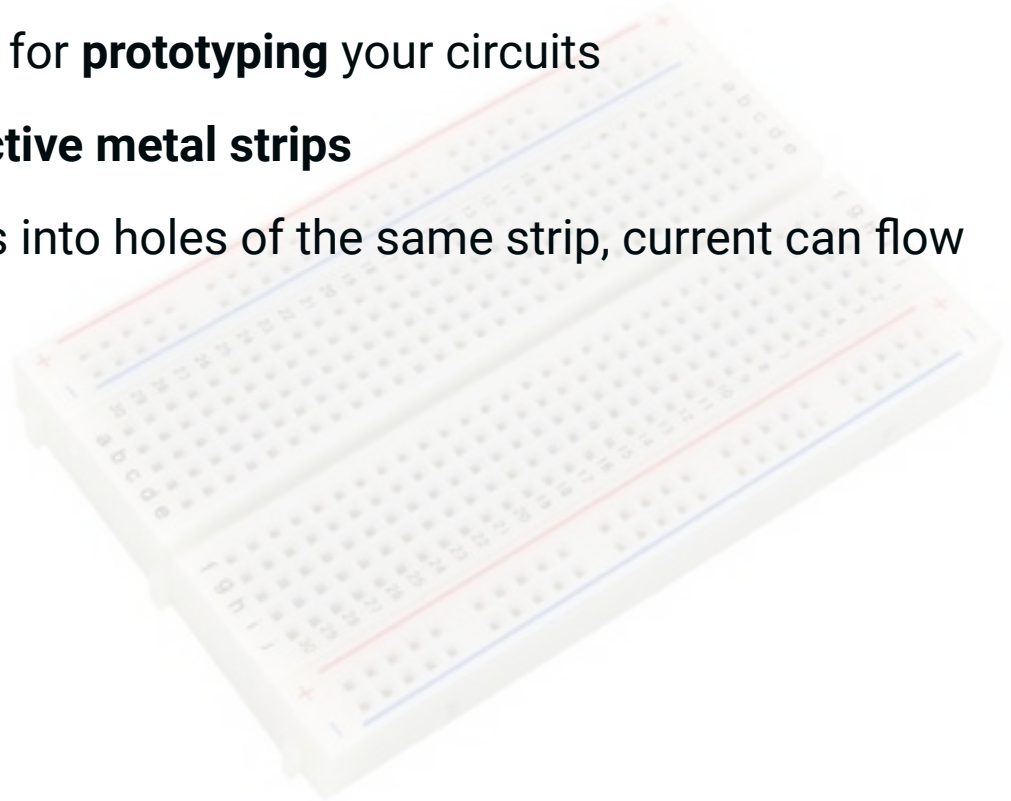- A **breadboard** is a reusable board for **prototyping** your circuits
- Inside the breadboard are **conductive metal strips**
 - When you insert components into holes of the same strip, current can flow between those components




Breadboards

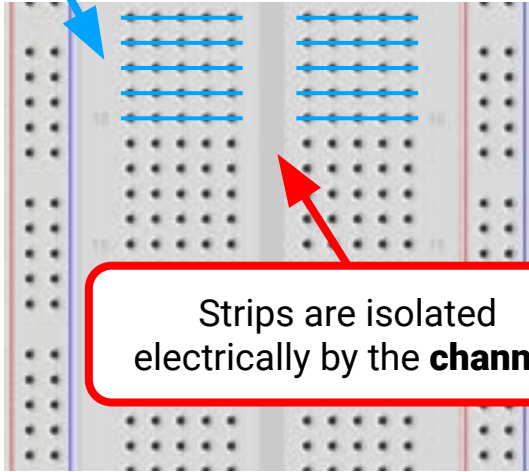Horizontal holes are electrically connected in a **strip**



Strips are isolated electrically by the **channel**

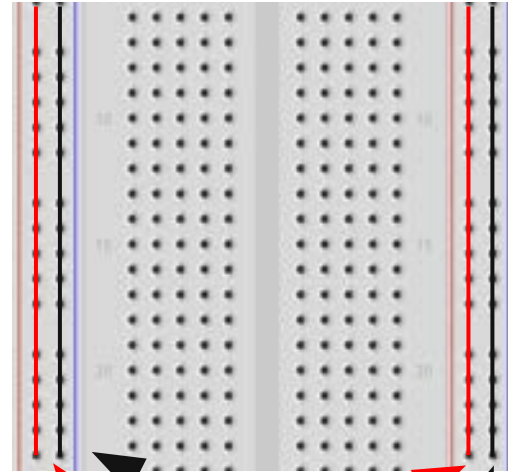Vertical strips are connected down the entire board



Power Rails

Ground Rails

+


-

Soldering

- Final circuit designs are often soldered onto **printed circuit boards (PCBs)** or **perfboards**
- **Soldering** is a process that joins circuit components together with a filler metal called **solder**



Printed Circuit Board

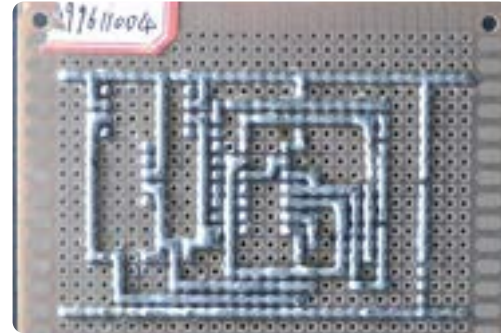


Perfboard

“In the matters of **soldering**, the **wide blade tip** is adequate for **removing components**. The **chisel-like, finer tip** is suited for **attaching components**. However, the **finest, most pointed tip** is to be **reserved for combat**.”

Miyamoto Musashi (circa 1620)

Famous Misquotes

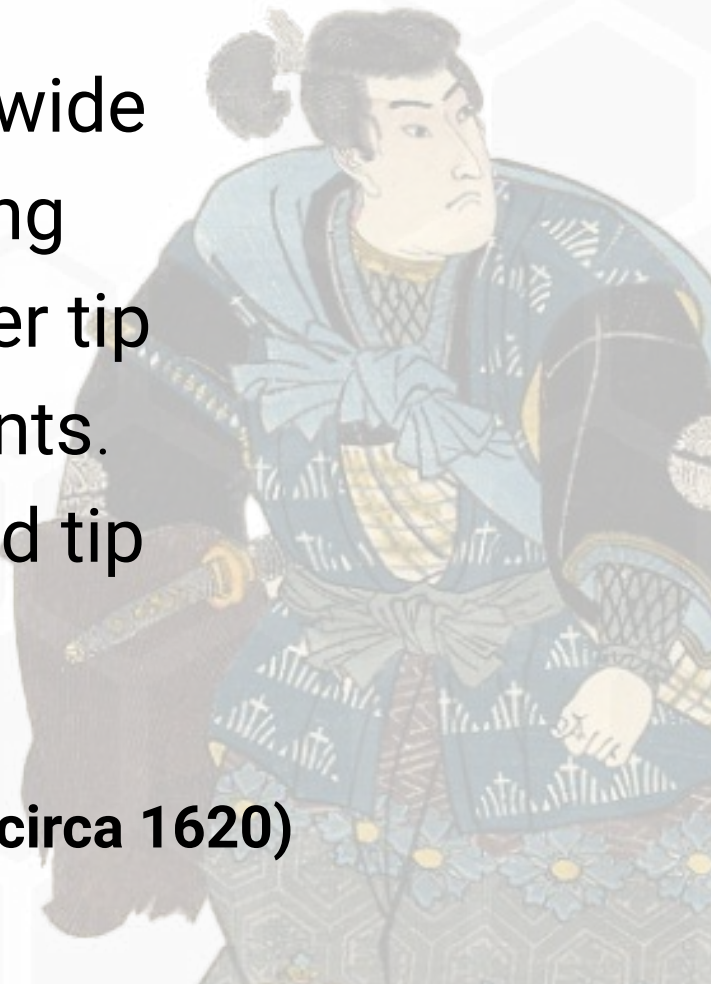

FAIR USE DISCLAIMER

Copyright Disclaimer under section 107 of the Copyright Act 1976, allowance is made for “fair use” for purposes such as criticism, comment, news reporting, teaching, scholarship, education and research.

Fair use is a use permitted by copyright statute that might otherwise be infringing.

Non-profit, educational or personal use tips the balance in favor of fair use.